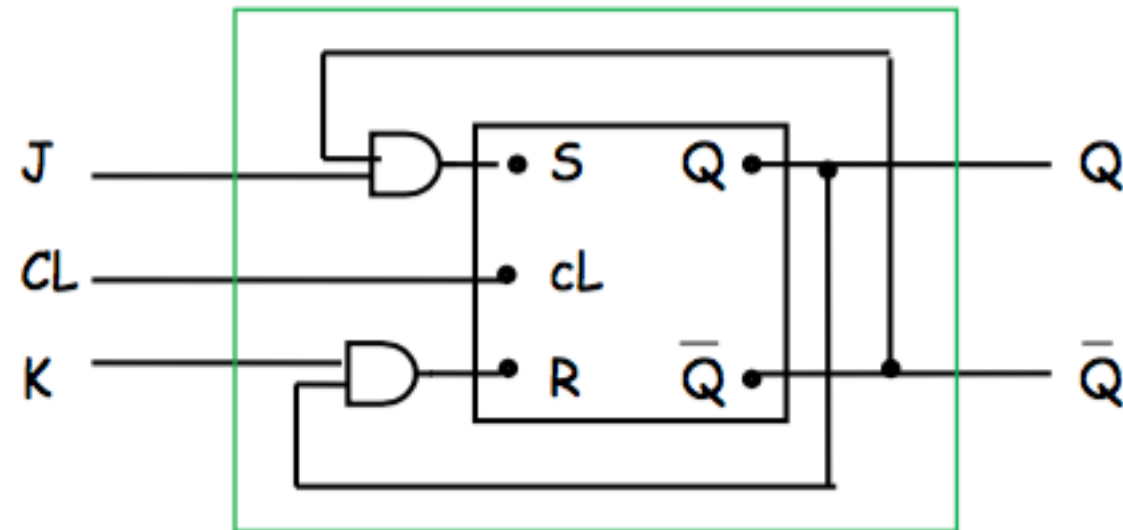


# Racing Problem

CLASS 20

## HW 21 - assigned

### J-K Flip-Flop



Describe its performance. For the truth table consider as inputs  $J$  and  $K$  only. Exclude the case  $J = K = 1$  from this truth table, and treat it separately.


# Shifting

Consider the diagram:

We initialize  $x_1 = x_2 = x_3 = 0$ . For IN we input the string of signals **IN** = 0, 1, 0, 0, 0, in sequence.

CL:

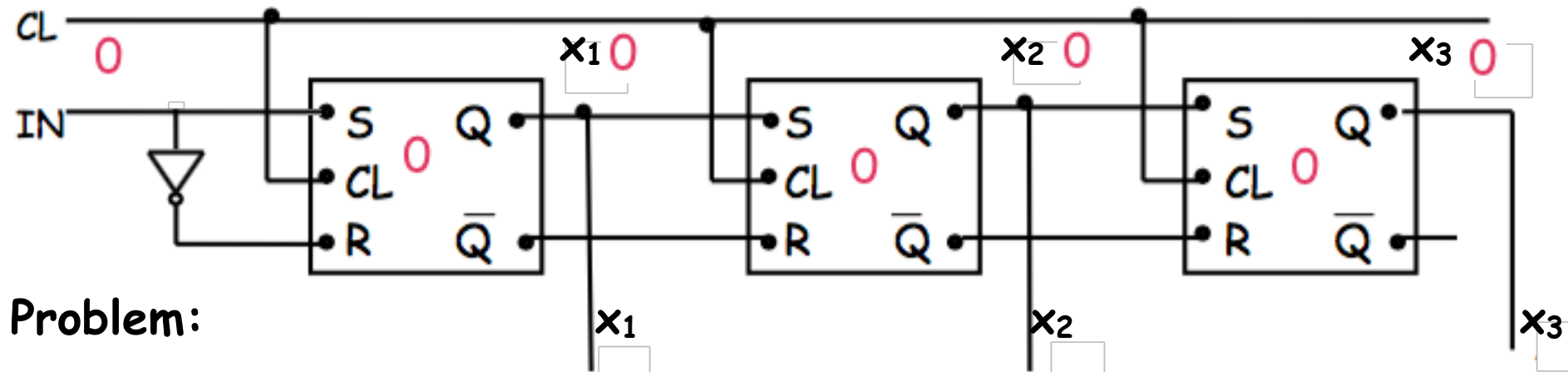It will allow us to see the shifting of the 1 as it progresses through  $x_1, x_2, x_3$ , in time.



## Racing Problem:

Instead of shifting, the signal 1 (or 0) may traverse the F-Fs too quickly: producing all outputs =1 (0) at same time. We will solve this problem later, and for now suppose it is solved, that is:

All S-R-CL Flop-Flops are such that the time needed for the signal to go through the Flip-Flop is greater than the time needed for CL to run the rising edge from 0V(=0) to 2V(=1) [when F-F enabled].

IN = 0


Time counts	CL	IN	X <sub>1</sub>	X <sub>2</sub>	X <sub>3</sub>
1	1	0	0	0	0
	0	0	0	0	0
2	1	1	0	0	0
	0	1	1	0	0
3	1	0	1	0	0
	0	0	0	1	0
4	1	0	0	1	0
	0	0	0	0	1
5	1	0	0	0	1
	0	0	0	0	0

These F-Fs are described the next slide, and have the racing problem solved:

The signal goes inside the F-F on phase 1 and out of F-F on phase 0 of CL

No change in outputs during phase 1 of CL.
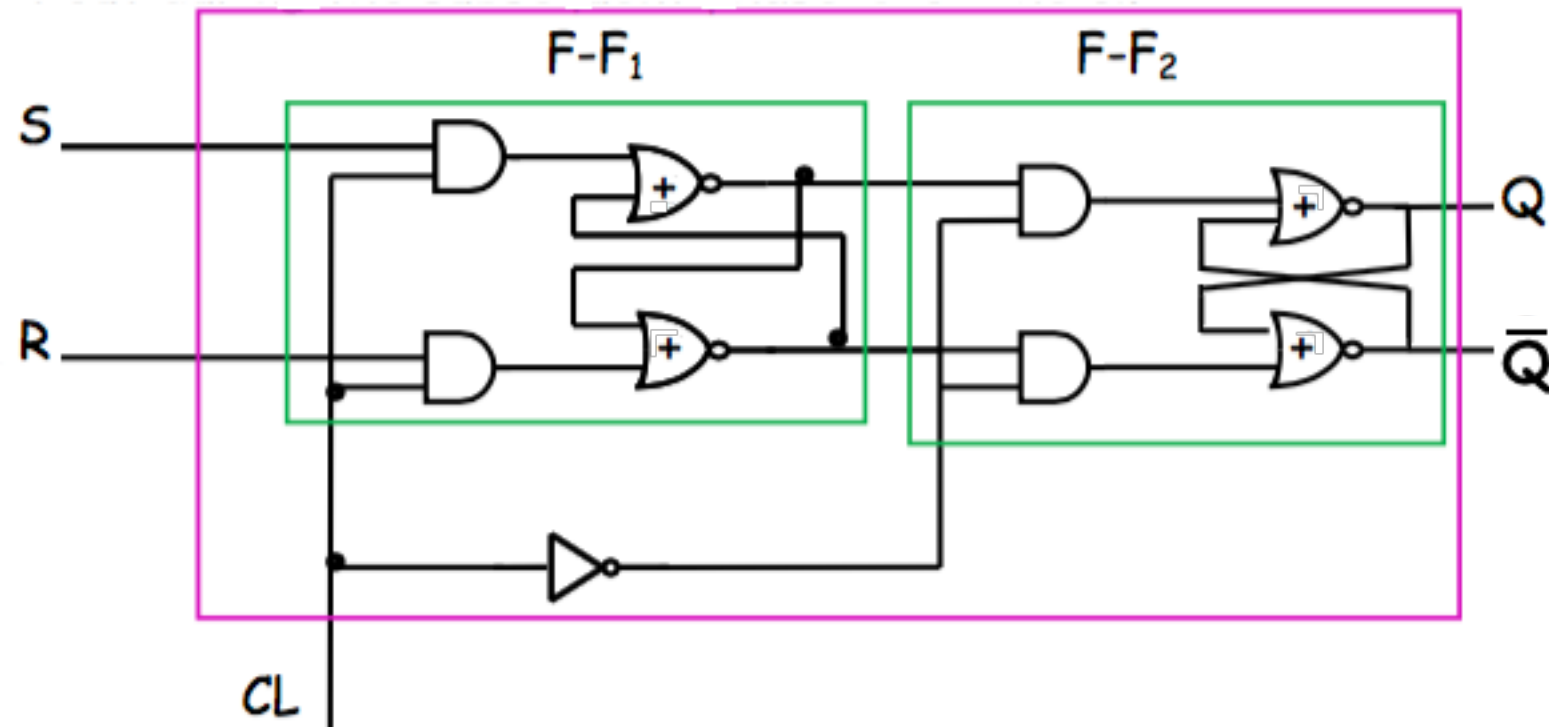
## Racing Problem Solution is the following F-F:



During the phase '1' of  $CL$ , the signal goes into the  $F-F_1$  but gets stuck in-between  $F-F_1$  and  $F-F_2$ , as  $F-F_2$  is not enabled. During the subsequent phase '0' of  $CL$ ,  $F-F_2$  gets enabled, and the signal gets finally through  $F-F_2$  and outputs the big F-F [ ☐ ].

The big F-F [ ☐ ] solves the 'Racing Problem'